

COL215P - Hardware Assignment 2

Machine Vision Through Neural Network Hardware

Submission Deadline: 30th September 2022

1 Introduction

This assignment is an exercise to implement machine vision through neural network hardware. We design a 3-layer Multi-layer Perceptron (MLP) for the vision task. The hardware, implemented on the Basys3 board, will take as input patterns from the *MNIST dataset*, and will classify it into one of 10 digit categories.

This assignment involves the design and integration of memories, registers, comparator, shifter and multiplier-accumulator components (MAC) in your design.

Please note that the diagrams in this document are for the illustration and explanation of the problem statement and do not represent the exact design to be implemented. The design choices can vary for each group and should be carefully explained in the report of the assignment.

2 Problem Description

Implement a 3-layer neural network inference in VHDL and test it on Basys3 board. Figure 1 shows an overview of the structure of the neural network with 3 layers: Input (28x28 or 1x784 when flattened), Hidden Layer 1 (1x64) and Output Layer (1x10). The network has been pre-trained on MNIST dataset. You will be provided with the pre-trained network parameters (Weights: 784x64 and 64x10, Biases: 64 and 10) in the form of a MIF file that can be loaded in Vivado. The description of how to use MIF file is given in Section 2.6.

 


Figure 1: 3-layer MLP pre-trained on MNIST dataset with int8 parameters and int16 activations. Network inference accuracy = 93%.

2.1 Operations performed in an MLP

The network shown in Figure 1 consists of all fully-connected layers in which all neurons between two layers are connected to each other. The operations in fully-connected layers are done using simple matrix-matrix multiplication or vector-matrix multiplication (which we will be doing in this assignment) as shown in Figure 2. Since these vectors and matrices could be very large, loading them from memory is extremely slow. It might sometimes be worth to load only a part of these matrices into a local memory instead of loading the complete matrix before starting the computation, as shown in Figure 2.

The overall design would consist of the following:

1. a Multiplier-Accumulator block (MAC): to perform vector-matrix multiplication
2. a Read-Write Memory (RWM, more popularly known as RAM or Random-Access Memory) - You will be using this memory to store outputs of all the layers

 


Figure 2: Vector-Matrix multiplication in a Fully-connected layer of MLP

3. a Read-Only Memory (ROM) - You will be using this memory to store the parameters and the input image
4. Registers - You will be using these to store temporary results across clock cycles
5. Comparator - You will be using a comparator to implement ReLU.
6. Shifter - You will be using this to perform integer division by a constant factor 32.
7. an overall circuit that stitches all modules to perform neural network inference on the given image.

 


Figure 3: Overview of the design implementation

Figure 3 shows a brief overview of the hardware implementation with control path and datapath. The datapath includes reading the inputs and parameters from a global memory (designed as RAM and ROM) and passing it over to the compute unit for computation. When the computation needs a large number of inputs at the same time, sometimes, another level of memory hierarchy is introduced in the design to store a part of the input. This concept was introduced in Figure 2. While the compute unit is working on the inputs already read in the local memory, the system can keep reading more inputs from the global memory in parallel. This helps to improve hardware utilization and improve performance with more parallelism.

The figure also shows a control path with 2 FSM's. One FSM controls the reading of inputs from global to local memory and another FSM controls the communication between local memory and compute. Figure 4 shows an overview of the control and data path taking an example of one set of inputs from one layer of the network.

2.2 Multiply-Accumulate block (MAC)

The first component to be designed in this assignment is a MAC unit that has a 16x8 multiplier, a register and a 16-bit adder to keep accumulating the products. Figure 5 shows the high-level overview of a multiplier-accumulate unit with the required input and output ports. For each layer you have to read an 8-bit weight and

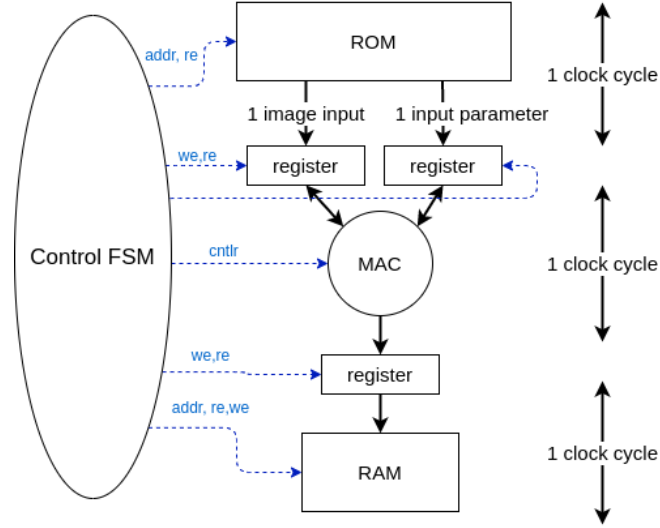


Figure 4: Overview of the control and data path for one set of inputs from one layer to generate one partial output

multiply it with a 16-bit input/activation (for the first layer please extend the 8-bit image input to 16-bits). The multiplier will generate a 24-bit output that can be truncated to 16-bits and sent to the adder for accumulation. After this, output will be scaled using a shifter 2.2.1 This way you will generate a 16-bit output activations at the end of each layer. This output will be stored in the RAM to be read as input to the next layer.

cntrl signal can be used to tell the unit whether it is the first product of the compute or not. If it is the first product, assign sum to the first product. After that the product needs to be accumulated with the previous sum. The other signals are self-explanatory.

 


Figure 5: Multiplier-Accumulate Unit

2.2.1 Shifter

To enabling storing of weights and bias in int8 format after training, the parameters are scaled up by factor of 32 for better precision. Therefore, during inference time division by factor of 32 will be done after performing multiplication and accumulation operation in int16. Division by 32 will be performed using down shifter as shown in figure 6. Kindly note down shifter can be placed inside MAC after accumulator, but that will require addition of control signal.

2.3 Memories

The design requires memories to store the inputs, temporary activations and the outputs of the networks. We will store the image, weights and biases in a read-only memory (ROM) and store the outputs and temporary data into a random-access memory (RAM).

 


Figure 6: Down shifter

 


Figure 7: RAM, ROM and Registers block diagram

2.3.1 Read-Only Memory or ROM

This memory will be used to store the following:

- Input Image: 28x28 image with each pixel of 8 bits or 1B. For storing the input we need 784 words, 8 bits wide. These will be stored at address 0 (0000_{16}) onwards.
- Weights and Biases: The network has total of 50816 weights and 74 biases of 8 bits each. For storing these, we need 50890 words, 8 bits wide. These will be stored at address starting from 1024 (0400_{16}).

2.3.2 Random-Access Memory or Read-Write Memory or RAM

This memory will be used to store the temporary activations (16-bit each) generated by each layer and the final output of the network. It will also be used to create the local memory mentioned earlier. **We leave it up to you to decide the size of the local memory needed.**

2.3.3 Registers

Registers are sequential elements that store temporary data across clock cycles in a multi-cycle design. The signal description is given in Figure 7. You can use these registers as per your design requirements.

2.3.4 Comparator

This block would be used to implement ReLU operation of the neural network.

2.4 Control Path

MLP execution is highly sequential and layer-wise. The control path is basically an FSM in your design which is supposed to do all the sequencing of the data required starting from generating addresses of the data in the order in which you want to read the data, generating the cycle-wise signals to be sent to the datapath to control the modules in the design.

2.5 Output

MNIST dataset has 10 classes (0-9). You need to run inference of the given image (28x28) on your design and display the output class number on one seven-segment display.

2.6 Using a MIF file in Vivado

Image, weight and bias parameter will be loaded into Vivado via MIF file. To read the MIF file, use `std.textio.all` in the code. Here is the sample function to read the MIF file and store the contents in the array. Add this function in your ROM VHDL module and call it to initialize the ROM.

The image is read from the MIF file and stored in flattened form into a vector *rom_block*. Use this vector to initialize the ROM module. Data in the MIF file is stored in ADDR:DATA form, where ADDR is 10 bits and DATA is 8 bits wide. Image pixel (x,y) will generate the address as $x \times (\text{column length}) + y$ in binary. E.g., if pixel is (2,2) then ADDR is: $2 \times 28 + 2 = 58$ (0000111010).

```
entity ROM_MEM is
  generic (
    ADDR_WIDTH      : integer := 10;
    DATA_WIDTH     : integer := 8;
    IMAGE_SIZE      : integer := 784;
    IMAGE_FILE_NAME : string := "imgdata.mif"
  );
end ROM_MEM;

architecture Behavioral of ROM_MEM is
  TYPE mem_type IS ARRAY(0 TO IMAGE_SIZE) OF std_logic_vector((DATA_WIDTH-1) DOWNT0 0);

  impure function init_mem(mif_file_name : in string) return mem_type is
    file mif_file : text open read_mode is mif_file_name;
    variable mif_line : line;
    variable temp_bv : bit_vector(DATA_WIDTH-1 downto 0);
    variable temp_mem : mem_type;
  begin
    for i in mem_type'range loop
      readline(mif_file, mif_line);
      read(mif_line, temp_bv);
      temp_mem(i) := to_stdlogicvector(temp_bv);
    end loop;
    return temp_mem;
  end function;
  // Signal declarations
  ...
  signal rom_block: mem_type := init_mem(IMAGE_FILE_NAME);
  ...

begin
  //Your ROM code
end Behavioral;
```

3 Submission and Demo Instructions

Since this assignment will span over 4 weeks, you will be evaluated every two weeks in the lab depending on your progress. We have broken down the design into blocks and you need to spend time accordingly to complete this assignment.

1. **Week 1 and Week 2:** Design and test all the sub-components of the datapath in the assignment. For this week, we are giving you a sample MIF file to get your memory block working. The actual image and weights would be uploaded later. You can test your ROM using this file. You can test your RAM using a testbench.
2. **Week 3 and Week 4:** Design the control path and integrate it with the data path. Test the design and show the class-output on seven-segment display.
3. Demo should be given in the assigned lab slot.

4. You are required to submit a zip file containing the following on Gradescope:
 - VHDL files for all the designed modules.
 - Simulated waveforms with test cases of each sub-component and complete design.
 - A short report (1-2 pages) explaining your approach. Include block diagram depicting the modules.
5. Post your doubts in Assignment 2 thread on Piazza.
6. Be ready with your design before the lab session. Validate the design through simulations. During the lab session, perform further validation of the design by downloading it into the FPGA board.

4 Resources references

- IEEE document: <https://ieeexplore.ieee.org/document/8938196>
- Basys 3 board reference manual: https://digilent.com/reference/_media/basys3:basys3_rm.pdf
- Online VHDL simulator: <https://www.edaplayground.com/x/A4>